

## ECSE 222 VHDL 2 Questions Report

Names:

Anja Kroon 260886624


Matt Zeitouni 260930709

1. Explain your VHDL Code.  
Please see the comments in our code.
2. Report the costs and the number of logic modules used to fit your designs on the FPGA board.


Task	1	2	3	4	5	6	7
Cost	72	100	25	25	N/A	N/A	22
Logic Utilization	2	2	2	2	4	4	2

3. Show representative simulation pilots of all tasks for all the possible input values (exhaustive test results). Note that you can simply include snapshots from the waveform that you obtained from EPWave. In order to fully capture all signals from the waveform, you can adjust the display range using the magnifier icons. Make sure that all signal names and axes are properly visible.

### Task 1: can\_SOP

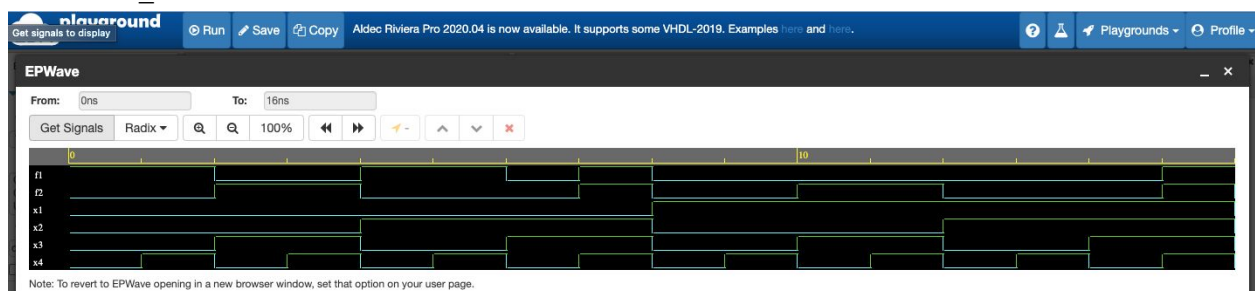


### Task 2: can\_POS

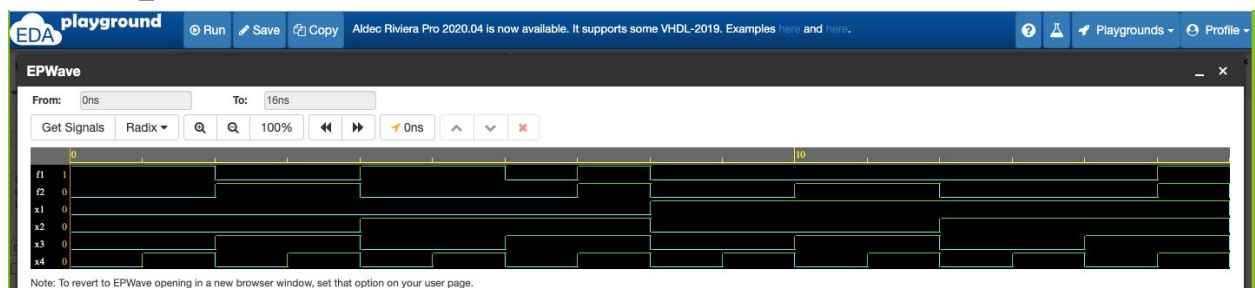


### Task 3: sim\_SOP


## ECSE 222 VHDL 2 Questions Report

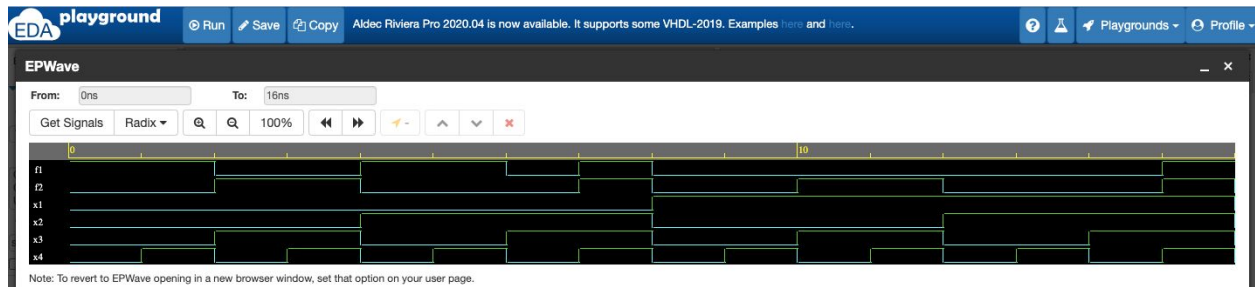


### Task 4: sim\_POS

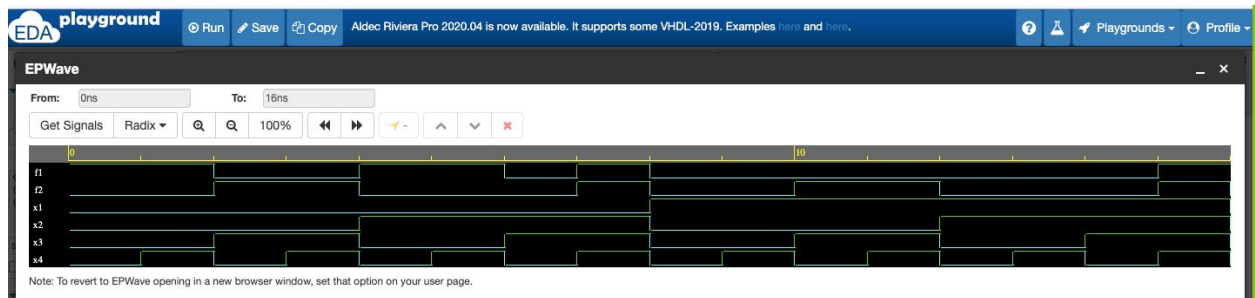


### Task 5: select\_assignment

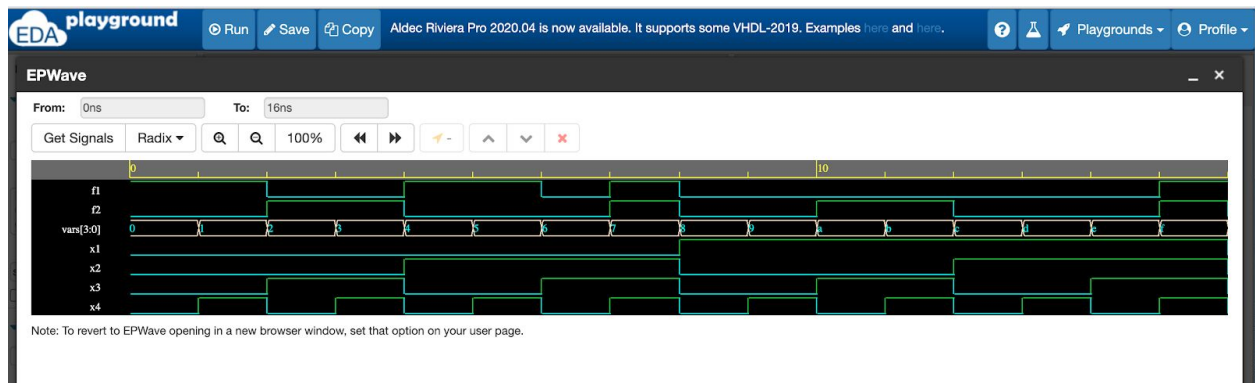

### Task 6: when\_assignment

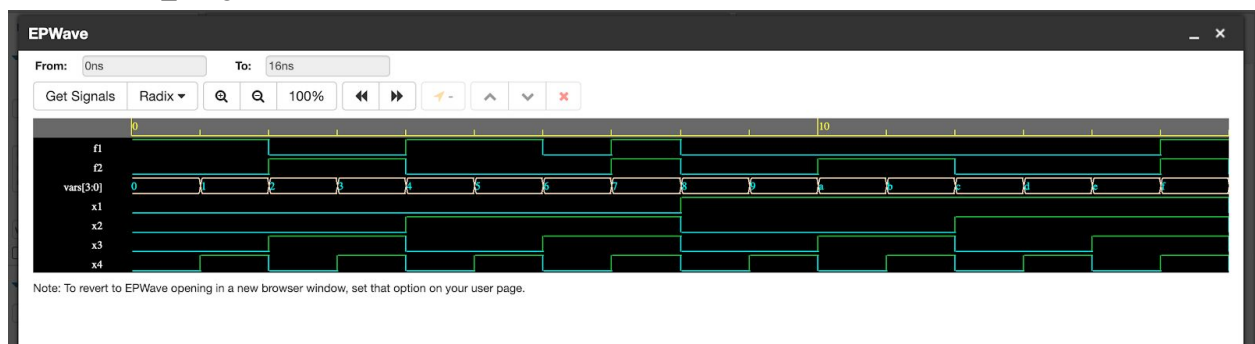

### Task 7: joint\_SOP

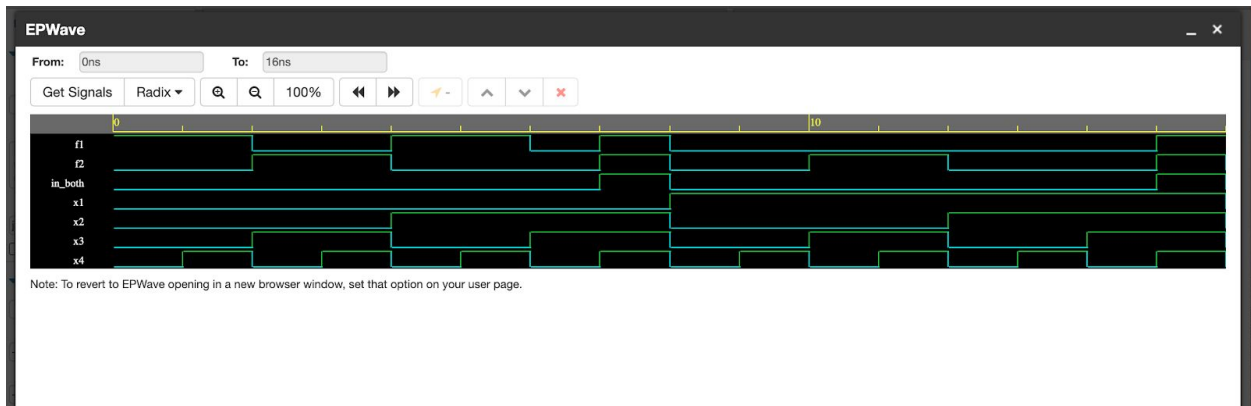

## For Part 1: Finding the canonical SOP

$x_1$	$x_2$	$x_3$	$x_4$	$f_1$	$f_2$
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	1	1

$$f_1 = \bar{x}_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 + \bar{x}_1 \bar{x}_2 \bar{x}_3 x_4 + \bar{x}_1 x_2 \bar{x}_3 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 x_4 + \bar{x}_1 x_2 x_3 \bar{x}_4 + \bar{x}_1 x_2 x_3 x_4$$

$$f_2 = \bar{x}_1 \bar{x}_2 x_3 \bar{x}_4 + \bar{x}_1 \bar{x}_2 x_3 x_4 + \bar{x}_1 x_2 x_3 \bar{x}_4 + x_1 \bar{x}_2 x_3 \bar{x}_4 + x_1 \bar{x}_2 x_3 x_4 + x_1 x_2 x_3 \bar{x}_4$$

As per the discussion board, we shall calculate cost as if  $f_1$  and  $f_2$  are in one circuit together but have two outputs.

$$\text{Cost} = +8 + (10)(5) + 14 = 50 + 8 + 14 = 72$$

$\uparrow$  complements       $\nwarrow$  10 distinct minterms       $\nwarrow$  7 for  $f_1$ , 7 for  $f_2$  to join together

## For Part 2: Finding the canonical POS

$x_1$	$x_2$	$x_3$	$x_4$	$f_1$	$f_2$
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	1	1

$$f_1 = (x_1 + x_2 + \bar{x}_3 + \bar{x}_4)(x_1 + x_2 + \bar{x}_3 + x_4)(x_1 + \bar{x}_2 + \bar{x}_3 + x_4)(\bar{x}_1 + x_2 + x_3 + x_4)(\bar{x}_1 + x_2 + x_3 + \bar{x}_4)(\bar{x}_1 + x_2 + \bar{x}_3 + x_4)(\bar{x}_1 + \bar{x}_2 + x_3 + x_4)(\bar{x}_1 + \bar{x}_2 + x_3 + \bar{x}_4)$$

$$f_2 = (x_1 + x_2 + x_3 + x_4)(x_1 + x_2 + x_3 + \bar{x}_4)(x_1 + \bar{x}_2 + x_3 + x_4)(x_1 + \bar{x}_2 + x_3 + \bar{x}_4)(\bar{x}_1 + \bar{x}_2 + x_3 + x_4)(\bar{x}_1 + \bar{x}_2 + x_3 + \bar{x}_4)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + x_4)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$$

$$\text{Cost} = +8 + (14)(5) + 22 = 100$$

$\uparrow$  complements

## For Part 3: simplified/optimized SOP

$x_3 x_4$	$x_1 x_2$		
1	1	0	0
1	1	0	0
0	1	1	0
0	0	0	0

$$f_1 = \bar{x}_1 \bar{x}_3 + x_2 x_3 x_4$$

3      4

3 + 4 for complements = 14

$$\text{cost} = 14$$

$x_3 x_4$	$x_1 x_2$		
0	0	0	0
0	0	0	0
1	1	1	1
1	0	0	1

$$f_2 = x_3 x_4 + \bar{x}_2 x_3$$

3      3

3 + 2 for complements = 14

$$\text{Total Cost} = 25$$

For Part 4: simplified / optimized POS

$x_3 x_4 \backslash x_1 x_2$	11	10	01	00
11	1	1	0	0
10	1	1	0	0
01	0	1	1	0
00	0	0	0	0

$$f_1 = (\bar{x}_1 + x_3)(x_2 + \bar{x}_3)(\bar{x}_3 + x_4)$$

$$\text{cost} = +4 + (3)(3) + 4 = 17$$

$\uparrow$  complements       $\uparrow$  maxterms       $\uparrow$  overall joining

$x_3 x_4 \backslash x_1 x_2$	11	10	01	00
11	0	0	0	0
10	0	0	0	0
01	1	1	1	1
00	1	0	0	1

$$f_2 = (x_3)(\bar{x}_2 + x_4)$$

$$\text{cost} = +2 + 3 + 3 = 8$$

$\uparrow$  complements       $\uparrow$  maxterms       $\uparrow$  overall joining

$$\text{Total Cost} = 17 + 8 = \underline{\underline{25}}$$

For Part 7: most joint-optimized SOP

$x_3 x_4 \backslash x_1 x_2$	11	10	01	00
11	1	1	0	0
10	1	1	0	0
01	0	1	1	0
00	0	0	0	0

$$f_1 = \bar{x}_1 \bar{x}_3 + x_2 x_3 x_4$$

Joint implementation:

$$f_1 = \bar{x}_1 \bar{x}_3 + x_2 x_3 x_4$$

$$f_2 = x_2 x_3 x_4 + \bar{x}_2 x_3$$

$$f_2 = x_2 x_3 x_4 + \bar{x}_2 x_3$$

$$\text{cost} = +4 + 3 + 3 + 3 + 3 + 6 = 22$$

$\uparrow$  shared       $\uparrow$   $f_2$        $\uparrow$   $f_1$        $\uparrow$  complements

$$\text{Cost} = \underline{\underline{22}}$$

$x_3 x_4 \backslash x_1 x_2$	11	10	01	00
11	0	0	0	0
10	0	0	0	0
01	1	1	1	1
00	1	0	0	1